

# Low Phase Noise CMOS Ring Oscillator VCOs for Frequency Synthesis

July 27, 1998

Rafael J. Betancourt Zamora and Thomas H. Lee


*Stanford Microwave Integrated Circuits Laboratory*


Paul G. Allen Center for Integrated Systems

Department of Electrical Engineering

Stanford University

<http://www-smirc.stanford.edu/>

 

 


## Outline

---

- ***Motivation***
- Phase Noise Theory
- Voltage-controlled Oscillator Design
- Conclusion and Acknowledgements



## What is Phase Noise?

 


- Undesirable phase fluctuations due to intrinsic device noise
- Output power is not concentrated at the carrier frequency alone
- Phase noise is represented as a ratio of power in 1Hz bandwidth in one sideband to the power of the carrier.
- Specified in dBc/Hz at a frequency offset from the carrier.



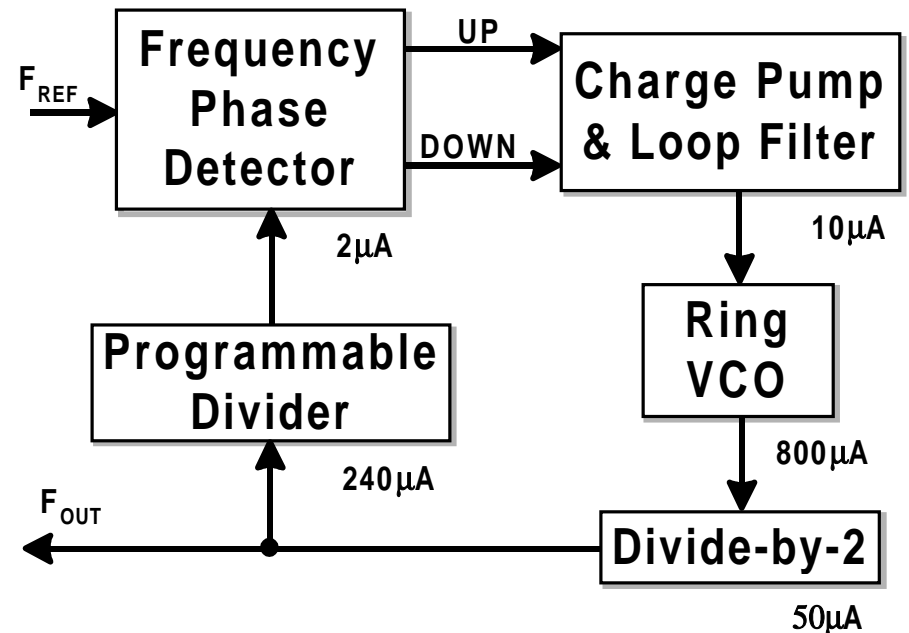
## Phase-locked Loops and Phase Noise

- Frequency synthesizers are implemented using phase-locked loops (PLLs).
- Major sources of power dissipation are the VCO and the frequency divider.
- Frequency reference is usually a crystal oscillator with very low phase noise.
- A PLL tracks phase noise of the reference within its loop bandwidth, relaxing the close-in phase noise requirements of the VCO.




Typical CMOS PLL frequency synthesizer<sup>1</sup>
 
<sup>1</sup>V. Kaenel, et al., "A 320MHz 1.5mW at 1.35V CMOS PLL for microprocessor clock generation," ISSCC, Feb. '96, pp.132-133.



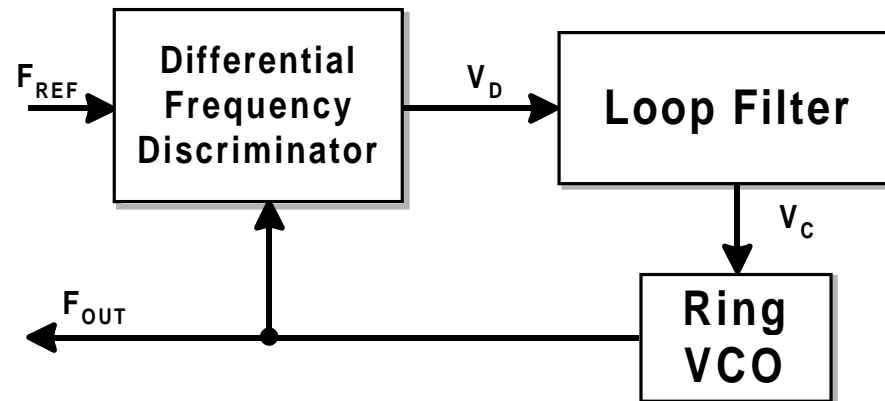
## Frequency-locked Loops and Phase Noise



FLL frequency synthesizer<sup>2</sup>

- A frequency-locked loop (FLL) synthesizer may not require a frequency divider.
- A FLL tracks frequency, not phase making close-in phase noise of VCO more critical.
- Biotelemetry application: 174-216MHz
 
<sup>2</sup>R.J. Betancourt-Zamora, A. Hajimiri, and T.H. Lee, "A 1.5mW, 200MHz CMOS VCO for wireless biotelemetry," First Int'l Workshop on Design of Mixed-Mode Integrated Circuits and Applications, Cancún, Mexico, pp. 72-74, July, 1997.




## Outline

---


- Motivation
- ***Phase Noise Theory***
- Voltage-controlled Oscillator Design
- Conclusion and Acknowledgements




## Oscillators are Time-Variant Systems

 

 - Current impulse injected at the peak changes the amplitude and has no effect on the phase.



 - Current impulse injected at zero-crossing changes the phase and has minimal effect on the amplitude.





### Phase Impulse Response

$$h_{\phi}(t, \tau) = \frac{\Gamma(\omega_0 \tau)}{q_{max}} u(t - \tau)$$

- Impulse Sensitivity Function  $\Gamma(x)$  is periodic.
- $q_{max}$  is the maximum charge displacement in the tank.



  
## Impulse Sensitivity Function for Ring Oscillators




$$\phi(t) = \frac{1}{q_{max}} \left[ \frac{c_o}{2} \int_{-\infty}^t i(\tau) d\tau + \sum_{n=1}^{\infty} c_n \int_{-\infty}^t i_n(\tau) \cos(n\omega\tau) d\tau \right]$$

 - $\Gamma(x)$  is calculated from the output waveform.
- $\Gamma(x)$  is expressed as a Fourier series and used to determine the phase noise resulting from noise sources.
- High sensitivity to noise at the transitions of the output





## Upconversion of Device $1/f$ Noise

 


- Phase noise close to the carrier results from the folding of device noise centered at integer multiples of the carrier frequency.
- Upconversion of device  $1/f$  noise occurs through  $\Gamma_{dc}$  the DC value of the ISF.
- $\Gamma_{dc}$  is governed by the symmetry properties of the waveform.



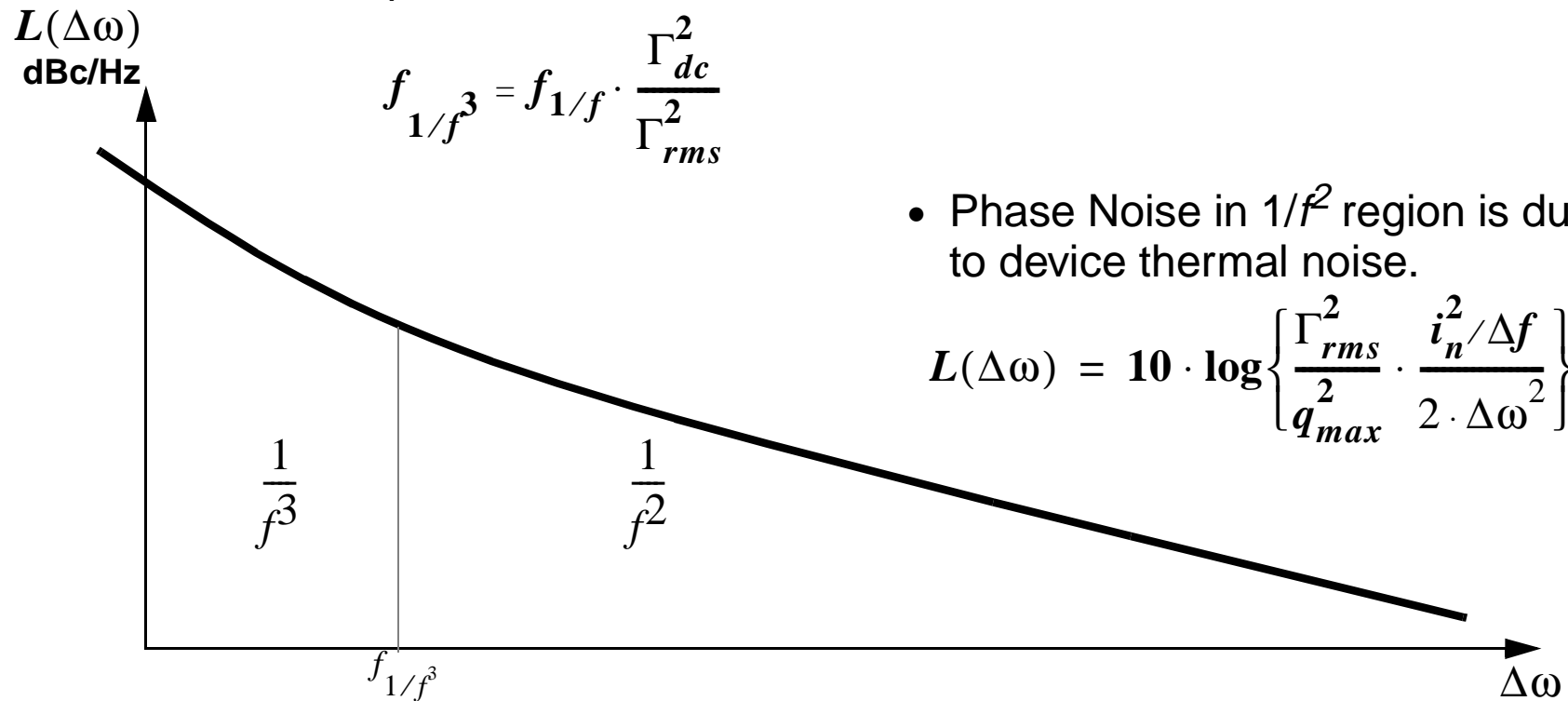
## Hajimiri Phase Noise Model<sup>3</sup>


- Phase Noise in  $1/f^3$  region is due to device  $1/f$  noise.
- It is commonly assumed that the  $1/f^3$  corner of phase noise is the same as the  $1/f$  corner of the device noise spectrum. This is NOT the case.


 
<sup>3</sup>A. Hajimiri and T.H. Lee, “A general theory of phase noise in electrical oscillators,” JSSC, vol. 33, pp. 179-194, Feb. 1998 (Correction in JSSC, vol. 33, p.928, June 1998).


 
## Calculation of $\Gamma_{rms}$ and $\Gamma_{dc}$ for Ring Oscillators<sup>4,5</sup>



$$\Gamma_{dc} = \frac{1}{2\pi} \int_0^{2\pi} \Gamma(x) dx$$

$$\Gamma_{rms}^2 = \frac{1}{2\pi} \int_0^{2\pi} \Gamma^2(x) dx$$

$$\frac{\Gamma_{dc}^2}{\Gamma_{rms}^2} = \frac{3}{2N} \cdot \frac{(1 - \beta)^2}{(1 - \beta + \beta^2)} \quad \beta = \frac{S_{rise}}{S_{fall}}$$

- S is the maximum slope of the normalized output waveform
- N is the number of stages

<sup>4</sup>A. Hajimiri, S. Limotyrakis and T.H.Lee, "Phase noise in multi-gigahertz CMOS ring oscillators," CICC, May '98, pp. 49-52


<sup>5</sup>A. Hajimiri, S. Limotyrakis and T.H.Lee, "Jitter and Phase Noise in Ring Oscillators," JSSC (submitted for publication)



 
## Outline

---


- Motivation
- Phase Noise Theory
- ***Voltage-controlled Oscillator Design***
- Conclusion and Acknowledgements



## Voltage-controlled Oscillator Design

 


- Use buffers with replica-feedback biasing.
- NMOS differential pairs with linear PMOS loads.
- $V_{ctl}$  changes the bias  $I_{dd}$  of the buffers.
- Replica bias ensures loads are mostly in their linear region by forcing the maximum single-ended swing  $V_s = V_{dd} - V_{ctl}$
- Frequency is controlled by changing the bias of the buffers and hence the delay through each cell.
- Power dissipation is determined by frequency and phase noise required.

 

## Power Dissipation of Differential Ring Oscillator

$$P \cong 2N^2 C_L V_{dd} V_s f$$

 


- $N$  is number of stages
- $C_L$  is total load capacitance at each buffer
- $V_s$  is maximum single-ended swing
- $V_{dd}$  is 3.3V


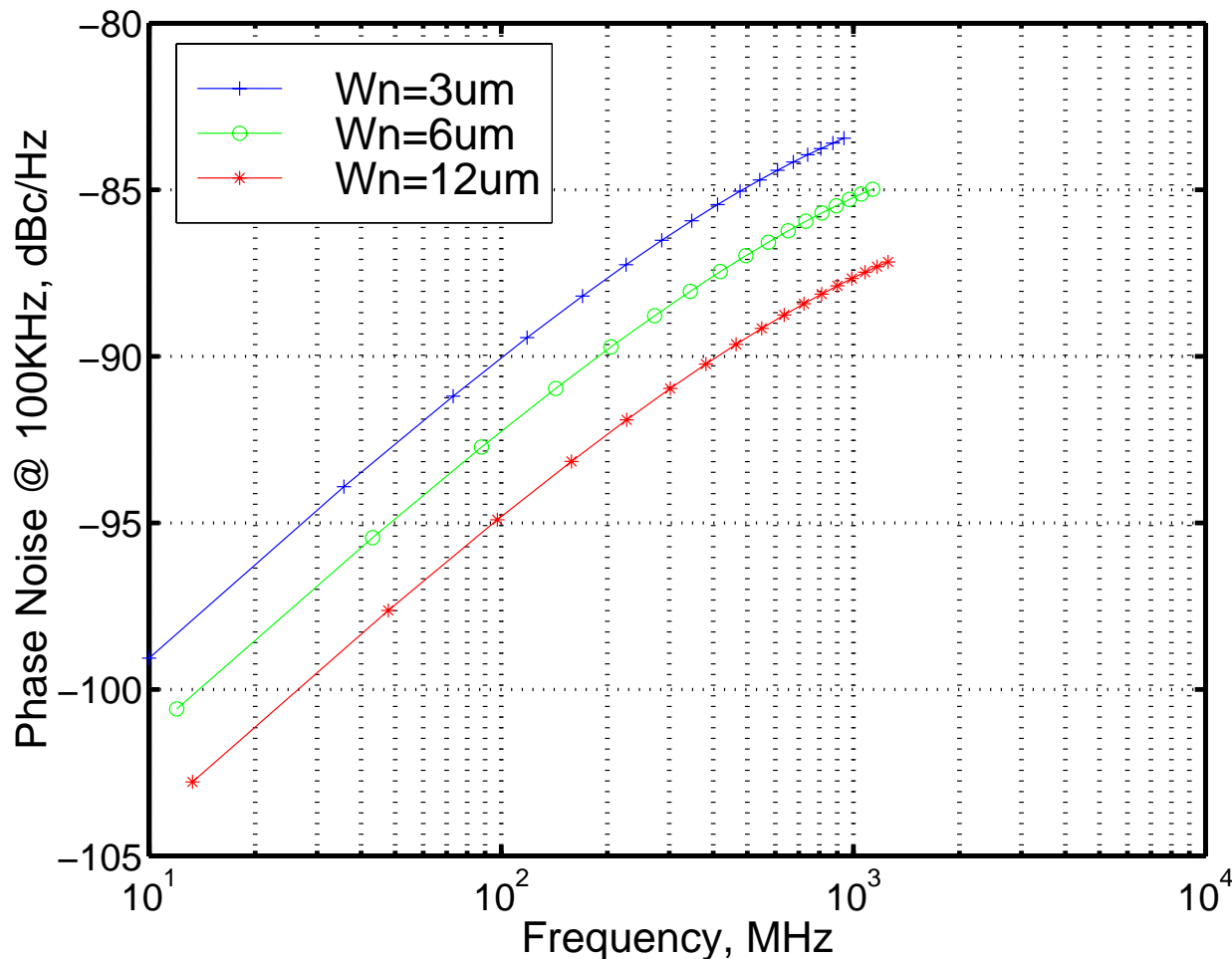
## Phase Noise of Differential Ring Oscillator

$$L\{\Delta f\} \geq \frac{18kTV_{dd}}{\pi^2 P} \cdot \left(\frac{2.5}{E_C L_{eff}} + 1\right) \cdot \left(\frac{f_o}{\Delta f}\right)^2 \cdot N$$


Lower bound on phase noise in the  $1/f^2$  region



- Minimum length short-channel differential pair devices
- $L_{eff} = 0.5 \mu\text{m}$
- $E_C = 5.6 \times 10^6 \text{V/m}$



## Phase Noise vs. Power Dissipation



 


**Selected  $W_n=6\mu m$  for 200MHz at 2.1dBm (1.6mW), -90dBc/Hz @ 100KHz**





## Differential Buffer Topology

   

### Clamped load

- Excellent supply rejection<sup>6</sup>.
- The cross-coupled loads make delay insensitive to common-mode noise.

### Symmetric load


- Good supply noise rejection.
- Used extensively in PLL and clock generators<sup>7</sup>.

### Cross-coupled load

- Sweep width of cross-coupling devices with fixed total width ( $W_1 + W_2 = W_3 = 6\mu m$ ) of the loads.
- Maximum symmetry for  $W_1 = W_2 = 0.5W_3$


<sup>6</sup>M. Horowitz, et al., "PLL design for a 500MB/s interface," ISSCC, Feb. 1993, pp. 160-161.
 
<sup>7</sup>J. Maneatis, "Low-jitter and process-independent DLL and PLL based on self-biased techniques," ISSCC, Feb. 1996, pp. 130-131, 430.


 
## Comparison of Phase Noise

- Assumed  $f_{1/f} = 3\text{MHz}$
- $1/f^2$  regions are within 2.6dB as expected for similarly sized noise sources.
- $1/f^3$  corner for cross-coupled load buffer is 20 times lower than that of the clamped load.
- Good agreement with measurements previously reported for clamped load



Oscillator	$1/f^3$ corner	L{100KHz}
(a) Clamped Load	137KHz	-75dBc/Hz
(b) Symmetric Load	36KHz	-77dBc/Hz
(c) Cross-coupled Load	6.5KHz	-80dBc/Hz



## Conclusions and Acknowledgements

---

- A design technique based on the Hajimiri model was presented for the design of low phase noise VCOs.
- We compared the phase noise performance of three differential buffer stages.
- We proposed a cross-coupled load buffer that achieves lower phase noise in the  $1/f^3$  region by exploiting single-ended symmetry in the oscillator's waveform.

- 
- This work was partially supported by NASA-Ames Research Center through a Training Grant No. NGT 2-52211.
  - We wish to thank Ali Hajimiri, and Miguel Gabino-Perez for their assistance.