




Noise Tutorial: Low-frequency CMOS Analog Design

May 16, 2002




Rafael J. Betancourt-Zamora

<http://www.betasoft.org/>

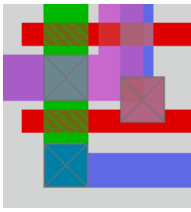


Outline

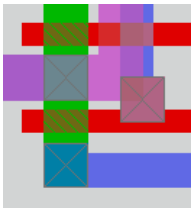- ***Goals***
- Noise Overview
- Resistor Noise Sources
- MOSFET Noise Sources
- Noise of Common Amplifier Topologies
- Examples
- Summary




Goals

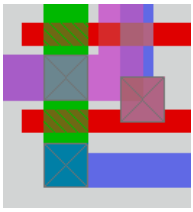- Grasp the importance of noise performance in low-frequency instrumentation design
- Understand the types of noise present in integrated resistors and MOS devices.
- Understand the noise trade-offs of different circuit topologies
- Perform simple noise analysis



Outline

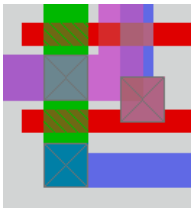- Goals
- ***Noise Overview***
- Resistor Noise Sources
- MOSFET Noise Sources
- Noise of Common Amplifier Topologies
- Examples
- Summary




What is noise?

- Unwanted disturbance that interferes with a desired signal
- External: power supply & substrate coupling, crosstalk, EMI, etc.
- Internal: random fluctuations that result from the physics of the devices or materials
- Smallest detectable signal, signal-to-noise ratio (SNR), and dynamic range are determined by noise


$$SNR = \frac{P_{signal}}{P_{noise}} = \frac{V_{rms, signal}^2}{V_{rms, noise}^2}$$

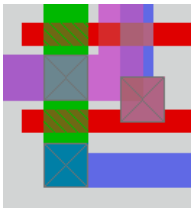We will look at internal noise sources and how they affect key performance metrics.




What does it look like?

WHITE NOISE (GAUSSIAN DISTRIBUTION)

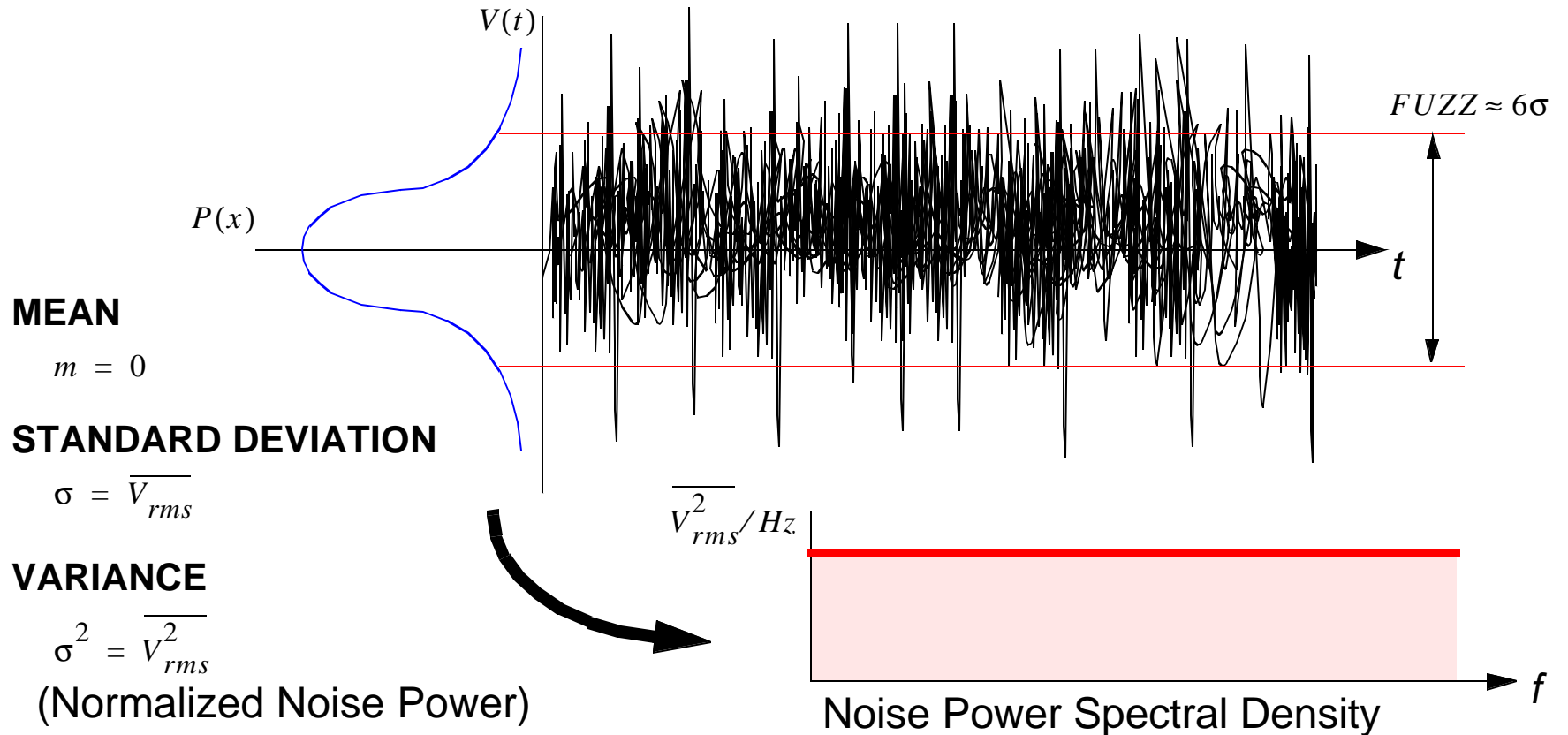

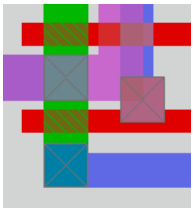
- Random process with zero mean
- Instantaneous amplitude is unpredictable
- Average noise power can be measured (variance)



Types of Noise

THERMAL


- thermal excitation of charge carriers

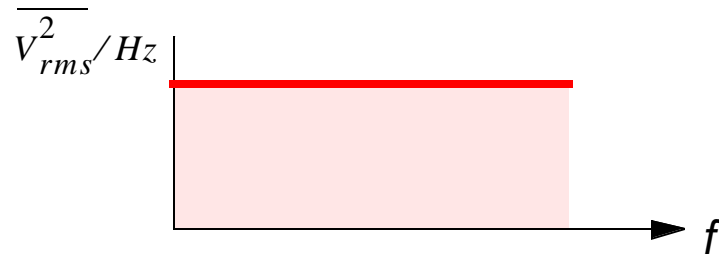

$$\frac{\overline{V_{rms}^2}}{\Delta f} = 4kTR, \text{V}^2/\text{Hz}$$

SHOT

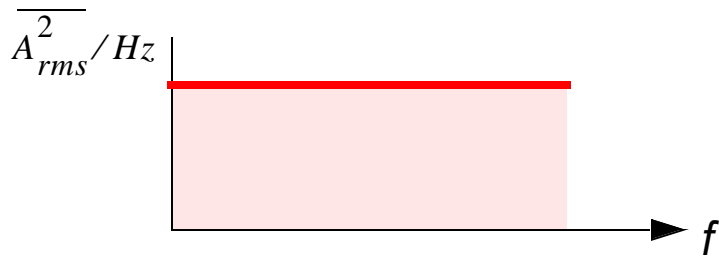
- fluctuations in dc current flow through junctions



$$\frac{\overline{I_{rms}^2}}{\Delta f} = 2qI_{DC}, \text{A}^2/\text{Hz}$$


FLICKER

- traps in semiconductors

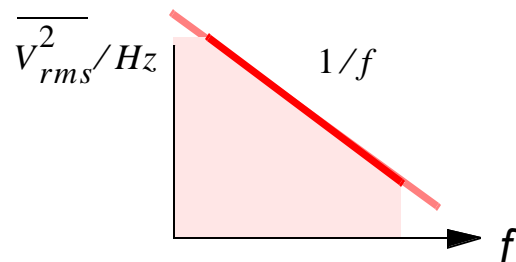


$$\frac{\overline{V_{rms}^2}}{\Delta f} = \frac{K_f \cdot V_{DC}^2}{f}, \text{V}^2/\text{Hz}$$

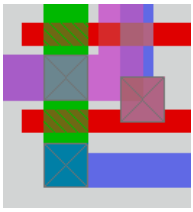T = Temperature, K
 k = 1.38×10^{-23} J/K
 q = 1.6×10^{-19} C
 K_f = Flicker coefficient





Outline

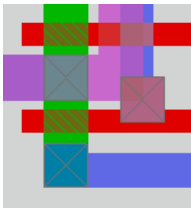- Goals
- Noise Overview
- ***Resistor Noise Sources***
- MOSFET Noise Sources
- Noise of Common Amplifier Topologies
- Examples
- Summary



Resistor Thermal Noise

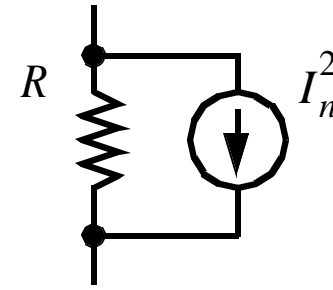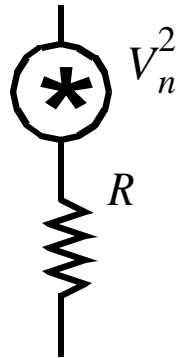

NOISE DENSITY $\frac{\overline{V_n^2}}{\Delta f} = 4kTR, V^2/\text{Hz}$

$\frac{\overline{I_n^2}}{\Delta f} = \frac{4kT}{R}, A^2/\text{Hz}$


NOISE POWER $\overline{V_n^2} = 4kTR\Delta fn, V^2$

$\overline{I_n^2} = \frac{4kT}{R}\Delta fn, A^2$


Δfn = NOISE BANDWIDTH

- Integrate noise PSD over frequency to arrive at total noise power.
- For white noise, multiply PSD by noise bandwidth.

1kΩ @ 25 °C
4.05 nV/√Hz
4.05 pA/√Hz

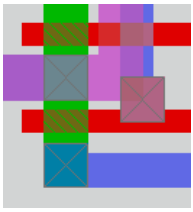


Noise Bandwidth

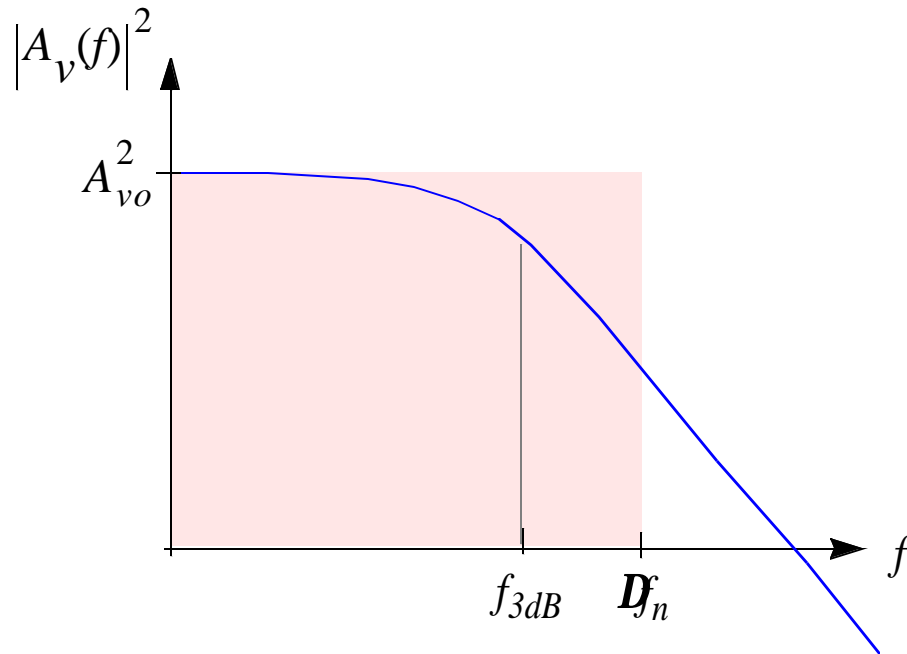


No. Poles	NOISE BW
1	$\Delta f_n = \frac{\pi}{2} \cdot \Delta f_{3dB}$
2	$\Delta f_n = 1.22 \cdot \Delta f_{3dB}$
3	$\Delta f_n = 1.16 \cdot \Delta f_{3dB}$
2nd-order BPF	$\Delta f_n = \frac{\pi}{2} \cdot \Delta f_{3dB}$

$$A_{vo}^2 \cdot \Delta f_n = \int_0^{\infty} |A_v(f)|^2 df$$

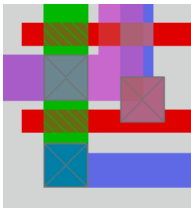- Noise bandwidth is defined for a brickwall transfer function
- Noise bandwidth is not the same as 3dB bandwidth



kT/C Limit

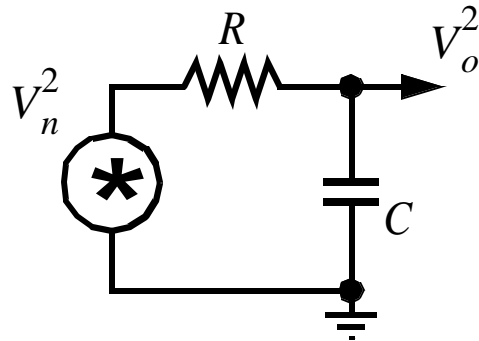


$$\overline{V_o^2} = 4kTR\Delta f_n, V^2$$

$$\overline{V_o^2} = 4kTR\left(\frac{1}{4RC}\right)$$

$$\left. \begin{aligned} \Delta f_n &= \frac{\pi}{2} \cdot \Delta f_{3dB} \\ \Delta f_{3dB} &= \frac{1}{2\pi RC} \end{aligned} \right\} \Delta f_n = \frac{1}{4RC}$$


$$\overline{V_o^2} = \frac{kT}{C}, V^2$$

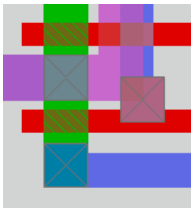- Total noise power is independent of R
- Capacitor is noiseless, but accumulates noise from resistor
- This fundamental limit is important for sampled systems




Combining Noise Sources

SERIES

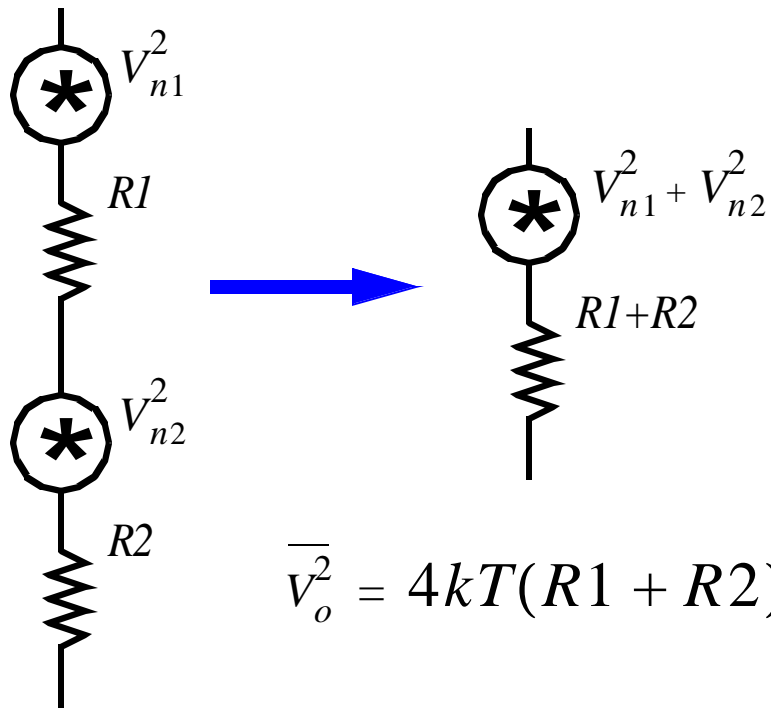

$$\overline{V_o^2} = 4kT(R1 + R2)\Delta fn$$

PARALLEL

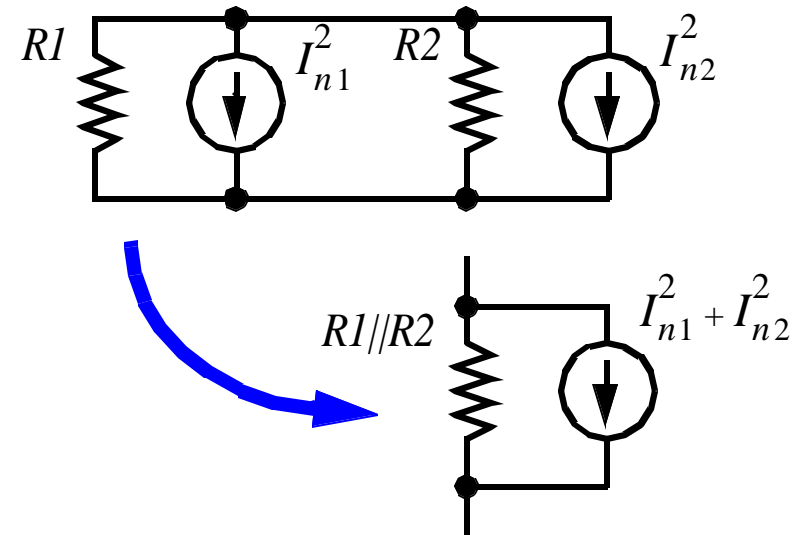


$$\overline{I_o^2} = 4kT\left(\frac{1}{R1} + \frac{1}{R2}\right)\Delta fn$$


- For uncorrelated noise sources, just add the noise powers.
- For correlated sources use:

$$V_o^2 = V_{n1}^2 + V_{n2}^2 + 2cV_{n1}V_{n2}$$

$|c| \leq 1$ **CORRELATION COEFFICIENT**

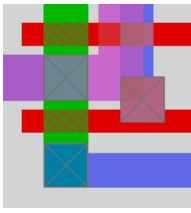

Resistor Flicker (1/f) Noise

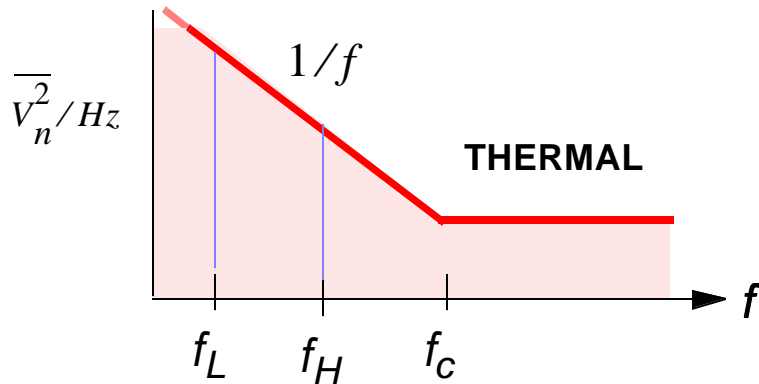

$$\frac{\overline{V_{nf}^2}}{\Delta f} = \frac{K_f \cdot V_{DC}^2}{f}, \text{ V}^2/\text{Hz}$$

$$\overline{V_{nf}^2} = \int_{f_L}^{f_H} \frac{K_f \cdot V_{DC}^2}{f} df = K_f \cdot V_{DC}^2 \ln\left(\frac{f_H}{f_L}\right), \text{ V}^2$$

$$\overline{V_{nf}^2} = 2.3 K_f \cdot V_{DC}^2 \text{ FOR } f_H/f_L = 10$$


- Constant noise power per decade
- f_c defines 1/f corner frequency where flicker noise is equal to thermal noise.

TOTAL RESISTOR NOISE

$$\overline{V_o^2} = 4kTR\Delta fn + K_f \cdot V_{DC}^2 \ln\left(\frac{f_H}{f_L}\right), \text{ V}^2$$

ASSUMES

$$\Delta fn \gg f_c$$

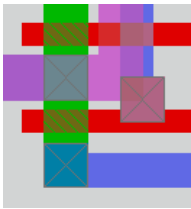

Noise Index

$$\left. \frac{\overline{V_{nf}^2}}{V_{DC}^2} \right|_{DEC} = \frac{K_f \cdot V_{DC}^2 \ln(10)}{V_{DC}^2} = 2.3K_f$$

$$NI = \sqrt{2.3K_f} \cdot 10^{-6}, \text{ mV/N/decade}$$


$$\overline{V_{nf}^2} = \frac{NI^2 \cdot V_{DC}^2}{2.3 \times 10^{-12}} \cdot \frac{1}{f}, \text{ V}^2/\text{Hz}$$

$$f_c = \frac{NI^2 \cdot V_{DC}^2}{2.3 \times 10^{-12} \cdot 4kTR}, \text{ Hz}$$

- Normalize $1/f$ noise per Volt, per decade of frequency
- Can express $1/f$ noise PSD and f_c in terms of NI


	$20 \log(NI)$
poly	-15dB
ndiff	-10dB
pdiff	-5dB

[Motchenbacher'93]

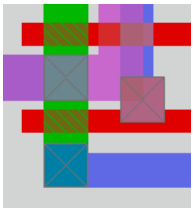

Outline

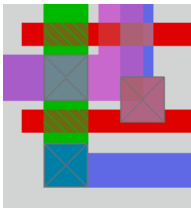- Goals
- Noise Overview
- Resistor Noise Sources
- ***MOSFET Noise Sources***
- Noise of Common Amplifier Topologies
- Examples
- Summary




Noise Sources in a MOSFET

DRAIN THERMAL NOISE

$$\overline{I_{nd}^2} = 4kT\gamma g_m, \text{ A}^2/\text{Hz}$$

$$\gamma = \begin{cases} 2/3, & \text{long channel} \\ 2-3, & \text{short channel} \end{cases}$$

- due to limited channel conductance

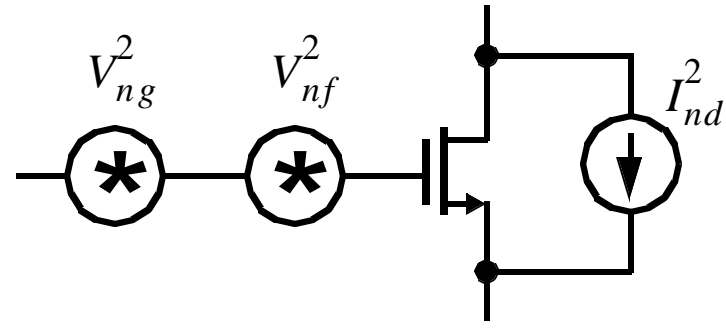

$R_{ds} = 1/g_m$
Long Channel
Saturation

GATE THERMAL NOISE

$$\overline{V_{ng}^2} = 4kTR_G/3, \text{ V}^2/\text{Hz}$$

- can be neglected with good layout

FLICKER NOISE

$$\overline{V_{nf}^2} = \frac{K_f}{WLC_{ox}f}, \text{ V}^2/\text{Hz}$$


FOR NMOS

$$K_f = 1.2 \times 10^{-24} \text{ V}^2 \cdot \text{F}$$


[Razavi'01]

SPICE
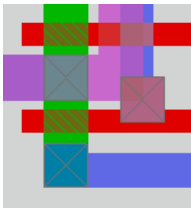
$$\overline{I_{nf}^2} = \frac{K_f \cdot I_{DC}^{AF}}{L_{EFF}^2 C_{ox} f}, \text{ A}^2/\text{Hz}$$



Input-referred Noise

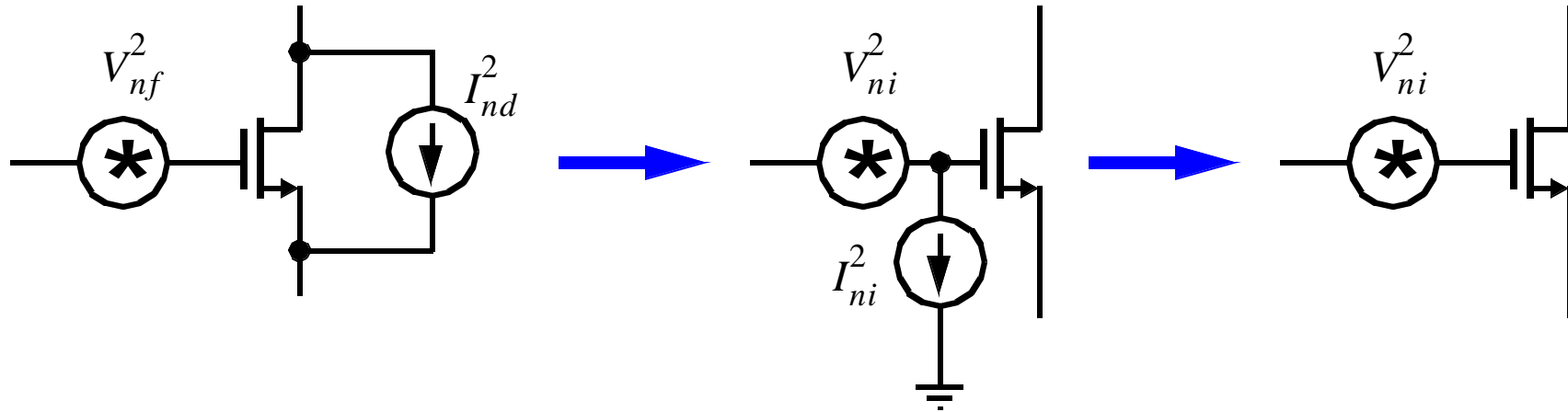


- Define equivalent input voltage and current noise sources.
- MOSFET input current noise source can be neglected at low frequencies.

INPUT-REFERRED DRAIN NOISE


$$\frac{\overline{V_{nd}^2}}{\Delta f} = \frac{\overline{I_{nd}^2}}{\Delta f} / g_m^2 = \frac{4kT\gamma}{g_m}, \text{ V}^2/\text{Hz}$$

TOTAL INPUT-REFERRED NOISE
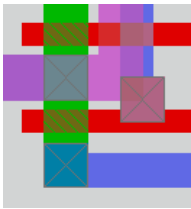
$$\frac{\overline{V_{ni}^2}}{\Delta f} = \frac{4kT\gamma}{g_m} + \frac{K_f}{WLC_{ox}f}, \text{ V}^2/\text{Hz}$$




1/f Corner Frequency

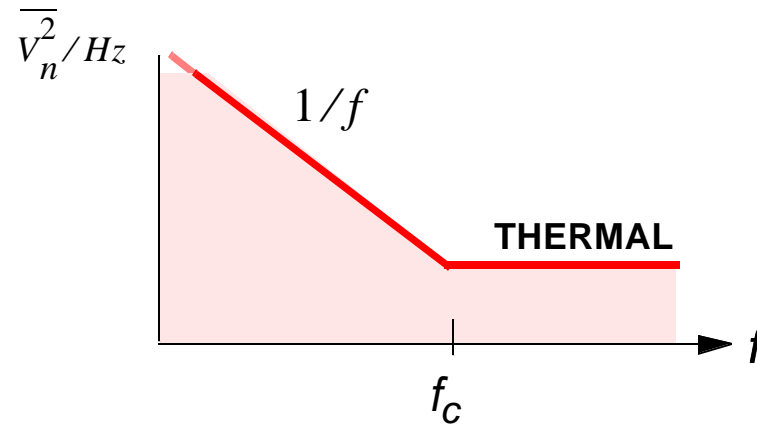

$$\frac{4kT\gamma}{g_m} = \frac{K_f}{WLC_{ox}f_c}$$


$$f_c = \frac{K_f \cdot g_m}{4kT\gamma WLC_{ox}}$$

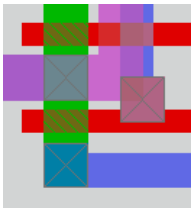- Defines where flicker noise is equal to thermal noise.
- Need to increase transistor area to reduce flicker noise.




Outline

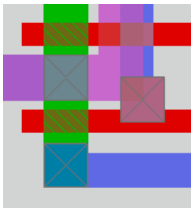- Goals
- Noise Overview
- Resistor Noise Sources
- MOSFET Noise Sources
- ***Noise of Common Amplifier Topologies***
- Examples
- Summary



Current Source

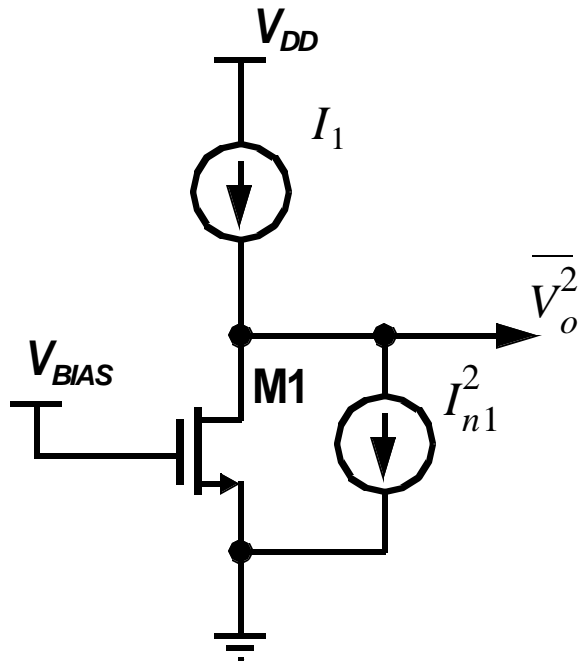


$$\overline{\frac{I_{n1}^2}{\Delta f}} = 4kT\gamma g_m, \text{ A}^2/\text{Hz}$$


$$\overline{\frac{V_o^2}{\Delta f}} = \overline{\frac{I_{n1}^2}{\Delta f}} \cdot r_o^2, \text{ V}^2/\text{Hz}$$

$$\overline{\frac{V_o^2}{\Delta f}} = 4kT\gamma g_m r_o^2, \text{ V}^2/\text{Hz}$$

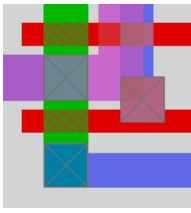- Neglected flicker noise of M1
- Need to minimize output current noise
- Minimize g_m for low noise



Common Source

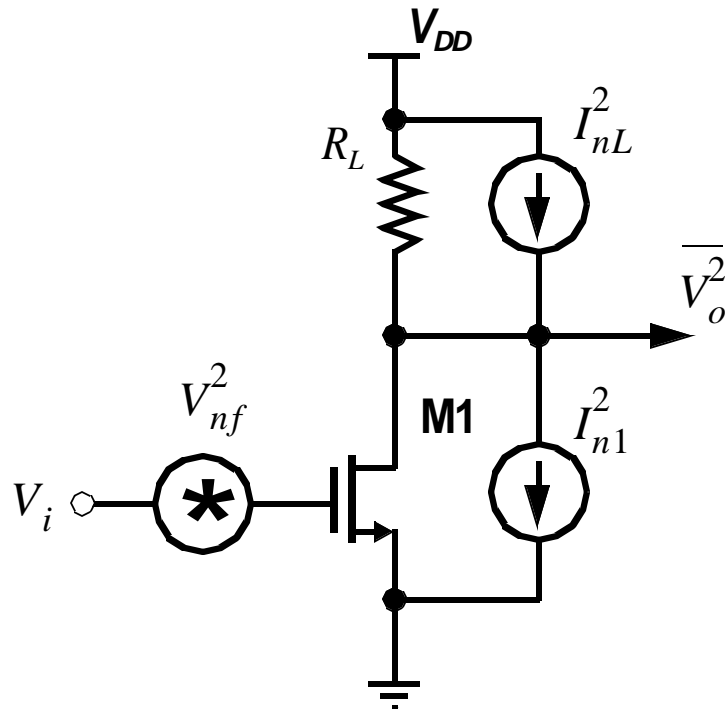


$$\overline{\frac{I_{n1}^2}{\Delta f}} = 4kT\gamma g_m, \text{ A}^2/\text{Hz}$$


$$\overline{\frac{I_{nL}^2}{\Delta f}} = \frac{4kT}{R_L}, \text{ A}^2/\text{Hz} \quad \overline{\frac{V_{nf}^2}{\Delta f}} = \frac{K_f}{WLC_{oxf}}, \text{ V}^2/\text{Hz}$$

$$\overline{\frac{V_{ni}^2}{\Delta f}} = \frac{4kT\gamma}{g_m} + \frac{K_f}{WLC_{oxf}} + \frac{4kT}{g_m^2 R_L}, \text{ V}^2/\text{Hz}$$

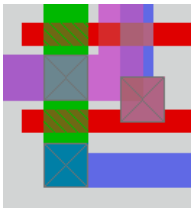- Neglected output conductance of M1
- Maximize g_m , R_L , and transistor area for low noise
- For a differential pair, double the noise



Source Follower

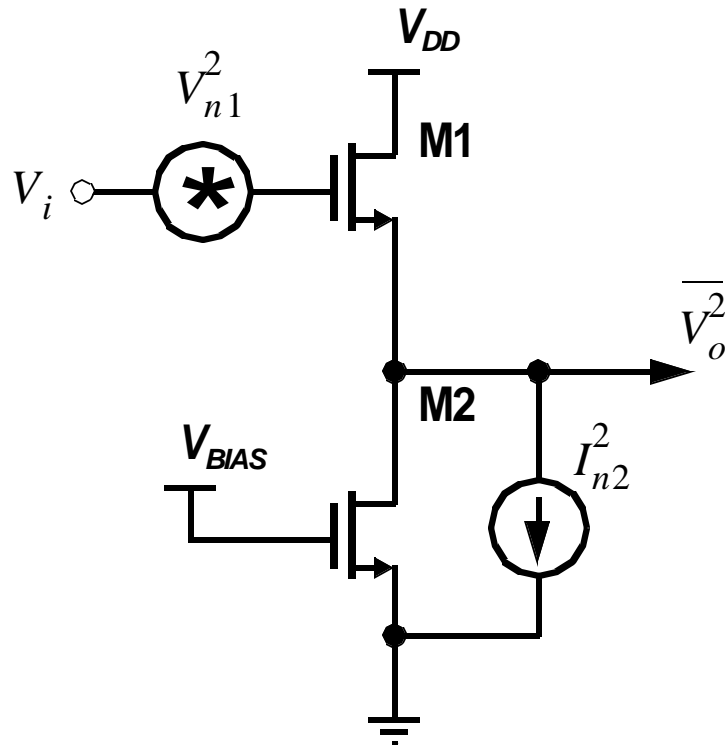


$$\frac{\overline{V_{n1}^2}}{\Delta f} = \frac{4kT\gamma}{g_{m1}} + \frac{K_f}{WLC_{ox}f}, \text{ V}^2/\text{Hz}$$

$$\frac{\overline{I_{n2}^2}}{\Delta f} = 4kT\gamma g_m, \text{ A}^2/\text{Hz}$$


$$\frac{\overline{V_{ni}^2}}{\Delta f} = \frac{\overline{V_{n1}^2}}{\Delta f} + \frac{\frac{\overline{I_{n2}^2}}{\Delta f} \cdot \left(\frac{1}{g_{m1}} \parallel r_{o1}^2 \parallel r_{o2}^2 \right)^2}{A_v^2}, \text{ V}^2/\text{Hz}$$

WHERE $A_v \approx 1$

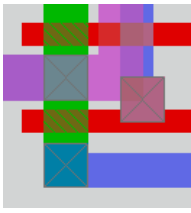- Neglected flicker noise of M2
- VERY NOISY, AVOID



Common Gate

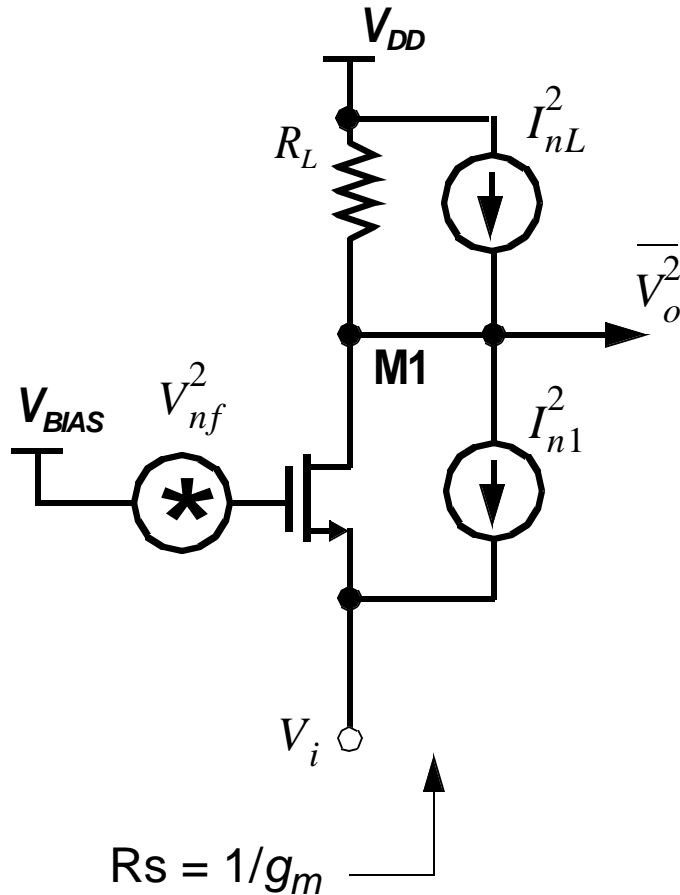

$R_s = 1/g_m$
(neglecting body effect)

$$\frac{\overline{I_{nL}^2}}{\Delta f} = \frac{4kT}{R_L}, \text{ A}^2/\text{Hz}$$


$$\frac{\overline{V_{nf}^2}}{\Delta f} = \frac{K_f}{WLC_{ox}f}, \text{ V}^2/\text{Hz}$$

$$\frac{\overline{I_{n1}^2}}{\Delta f} = 4kT\gamma g_m, \text{ A}^2/\text{Hz}$$


$$\frac{\overline{V_{ni}^2}}{\Delta f} = \frac{4kT\gamma}{g_m} + \frac{4kT}{g_m^2 R_L} + \frac{K_f}{WLC_{ox}f}, \text{ V}^2/\text{Hz}$$

$$\frac{\overline{I_{ni}^2}}{\Delta f} = \frac{4kT}{R_L} + \frac{g_m^2 K_f}{WLC_{ox}f}, \text{ A}^2/\text{Hz}$$

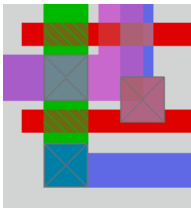- Neglected output conductance of M1
- Define equivalent input voltage and current noise sources
- Input noise current cannot be ignored
- Transfers load current noise to the input



Cascode

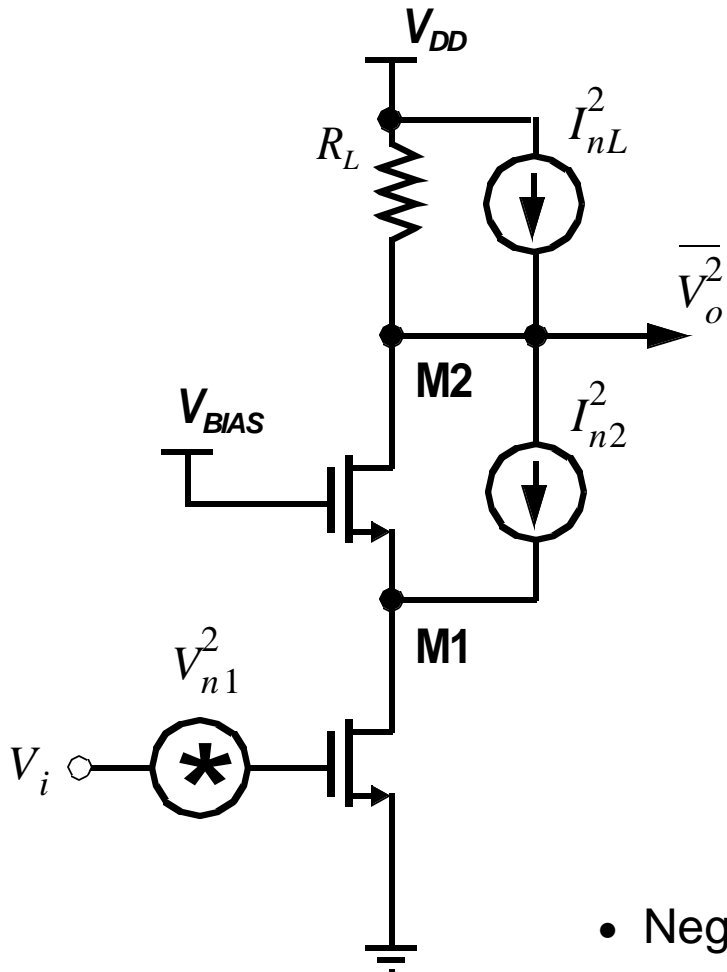


$$\overline{\frac{V_{n1}^2}{\Delta f}} = \frac{4kT\gamma}{g_{m1}} + \frac{K_f}{WLC_{ox}f}, \text{V}^2/\text{Hz}$$

$$\overline{\frac{I_{nL}^2}{\Delta f}} = \frac{4kT}{R_L}, \text{A}^2/\text{Hz}$$


$$\overline{\frac{V_{ni}^2}{\Delta f}} = \frac{4kT\gamma}{g_{m1}} + \frac{K_f}{WLC_{ox}f} + \frac{4kT}{g_{m1}^2 R_L}, \text{V}^2/\text{Hz}$$

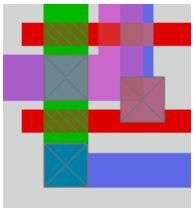- Neglected output conductance of M1
- M2's noise contribution is negligible at low frequencies
- Capacitance at M1's drain increase noise at high frequencies




Outline

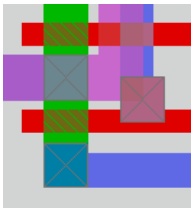- Goals
- Noise Overview
- Resistor Noise Sources
- MOSFET Noise Sources
- Noise of Common Amplifier Topologies
- ***Examples***
- Summary



Variable Resistor

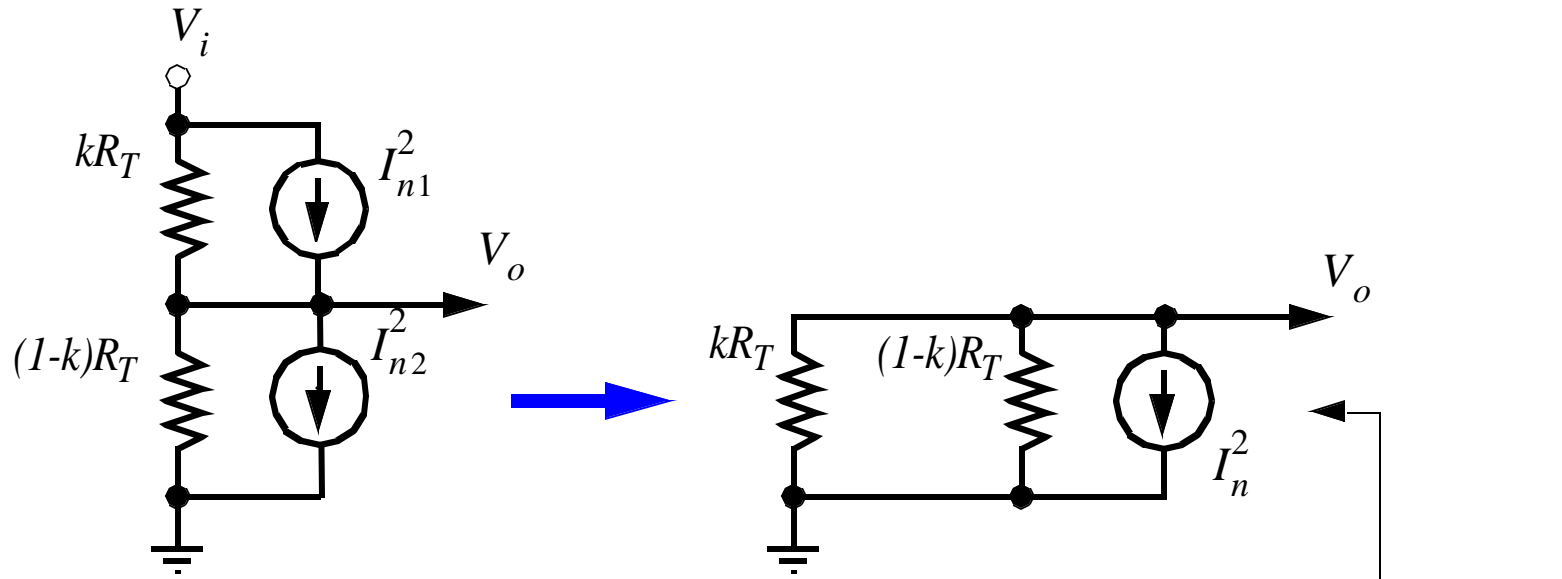


WORST CASE

$$k = 0.5$$


$$R_{eq} = R_T/4$$

$$\frac{\overline{I_n^2}}{\Delta f} = \frac{4kT}{R_{eq}}, \text{ A}^2/\text{Hz}$$
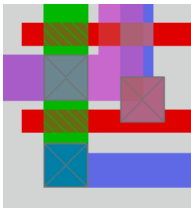
$$\frac{\overline{I_n^2}}{\Delta f} = \frac{16kT}{R_T}, \text{ A}^2/\text{Hz}$$



Inverting Operational Amplifier Filter

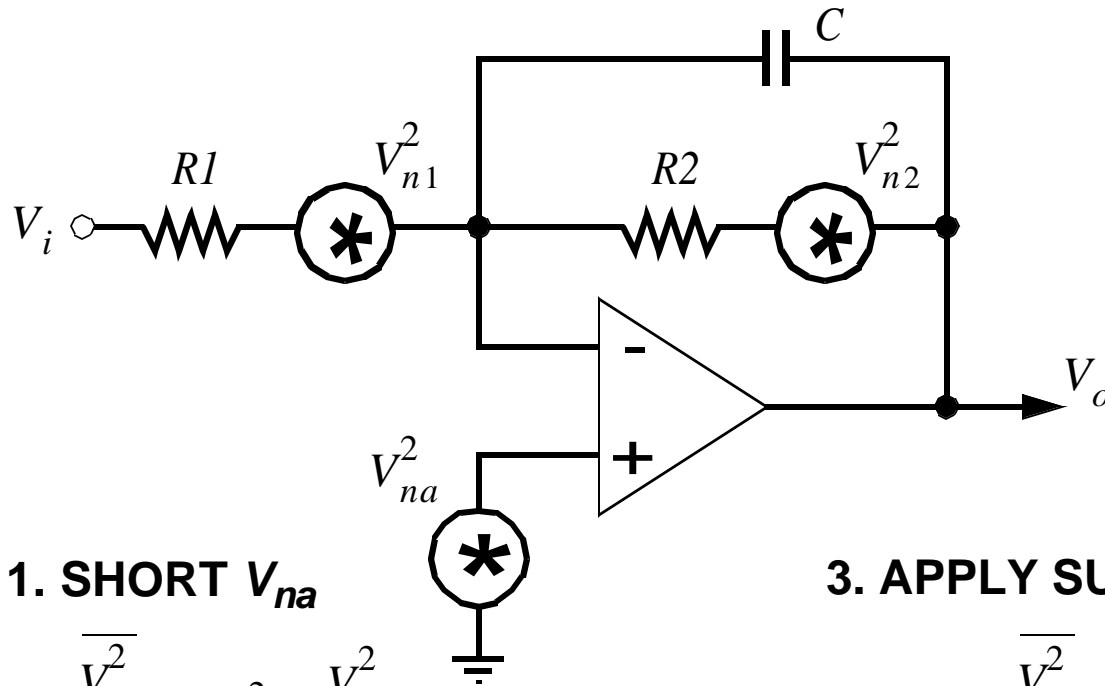

- Negligible input noise current
- Ignore 1/f noise
- Low frequency operation

where

$$A_{vi} = -\frac{R2}{R1} \quad A_{vni} = 1 + \frac{R2}{R1}$$

$$\Delta f_n = \frac{\pi}{2} \cdot \frac{1}{2\pi R2 C} = \frac{1}{4R2 C}$$

1. SHORT V_{na}

$$\frac{\overline{V_{ni}^2}}{\Delta f} = V_{n1}^2 + \frac{V_{n2}^2}{A_{vi}^2}$$

2. SHORT V_i


$$\frac{\overline{V_{ni}^2}}{\Delta f} = V_{na}^2 \left(\frac{A_{vni}^2}{A_{vi}^2} \right) = V_{na}^2 \left(1 + \frac{R1}{R2} \right)^2$$

3. APPLY SUPERPOSITION

$$\frac{\overline{V_{ni}^2}}{\Delta f} = V_{n1}^2 + \frac{V_{n2}^2}{A_{vi}^2} + V_{na}^2 \left(1 + \frac{R1}{R2} \right)^2$$


FOR LARGE GAIN, $R2 \gg R1$
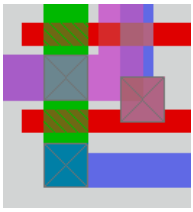
$$\frac{\overline{V_{ni}^2}}{\Delta f} = V_{n1}^2 + \frac{V_{n2}^2}{A_{vi}^2} + V_{na}^2, \text{ V}^2/\text{Hz}$$




Outline

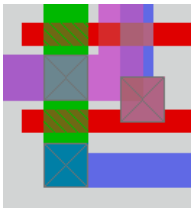- Goals
- Noise Overview
- Resistor Noise Sources
- MOSFET Noise Sources
- Noise of Common Amplifier Topologies
- Examples
- ***Summary***



What We Learned

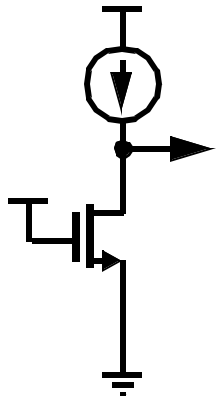


NOISE IN GENERAL

- Thermal noise and flicker noise are the major sources of headaches for low-noise, low frequency instrumentation design in CMOS.
- Noise bandwidth is not the same as 3dB bandwidth.
- Capacitors are noiseless, but they can accumulate noise.
- Resistors can have flicker noise, but only when there is current flow.

NOISE IN MOSFETS

- Need to increase transistor area to reduce flicker noise.
- Current source: Minimize g_m for low noise current
- Common source: Maximize g_m , R_L , and transistor area for low noise
- Source follower: VERY NOISY, AVOID
- Common gate: Transfers load current noise to the input. Input noise current cannot be ignored.
- Cascode: Cascode transistor noise contribution is negligible at low frequencies.

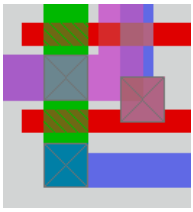

References

1. P.H. Garret, “Analog I/O Design: Acquisition, Conversion, Recovery,” *Reston Publishing, Reston, VA*, pp. 264, 1981.
2. D.A. Johns, K. Martin “Analog Integrated Circuit Design,” *John Wiley & Sons*, pp. 706, 1997.
3. C.D. Motchenbacher, J.A. Connelly, “Low Noise Electronic System Design,” *John Wiley & Sons*, pp. 422, 1993.
4. B. Razavi, “Design of Analog CMOS Integrated Circuits,” *McGraw-Hill*, pp. 684, 2001.